


HW3

1. Design a circuit that takes three bits (X_2, X_1, X_0) as input and produces one bit (O) as output. O is 1 if and only if the number of ones in X_2, X_1 , and X_0 is two or more.

a.

X_0	X_1	X_2	O
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 b. $\overline{x_0} \cdot x_1 \cdot x_2 + x_0 \cdot \overline{x_1} \cdot x_2 + x_0 \cdot x_1 \cdot \overline{x_2} + x_0 \cdot x_1 \cdot x_2$



c.

2.

a. $((A \cdot \overline{B}) \cdot B \cdot (B + \overline{C})) \cdot D$

b.

A	B	C	D	E
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

c. Propagation delay: 65ns

Critical path is from B through NOT then AND then NOT then AND then OR gates

3. Design a comparator that takes four bits (A1, A0, B1, B0) as input and produces one bit (O) as output. O is 1 if and only if the binary value of A1A0 is less than the B1B0 when both pairs of bits are interpreted as 2-bit unsigned integers.

a.


A0	A1	B0	B1	O
0	0	0	0	0
0	0	0	1	0

0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

b.

c. $\overline{A0} \cdot A1 \cdot \overline{B0} \cdot \overline{B1} + A0 \cdot \overline{A1} \cdot B0 \cdot \overline{B1} + \overline{A0} \cdot A1 \cdot B0 \cdot \overline{B1} + A0 \cdot A1 \cdot \overline{B0} \cdot \overline{B1} + A0 \cdot A1 \cdot \overline{B0} \cdot B1 + A0 \cdot A1 \cdot \overline{B0}$

 4. A JK flip-flop receives a clock and two inputs, J and K. On the rising edge of the clock, it updates its output, Q. If J and K are both 0, Q retains its old value. If only J is 1, Q becomes 1. If only K is 1, Q becomes 0. If both J and K are 1, Q becomes the opposite of its present state. Construct a JK flip-flop using a D flip-flop and some additional combinational logic.



a.

b. $\bar{J} \cdot \bar{K} \cdot Q + \bar{J} \cdot K \cdot \bar{Q} + J \cdot \bar{K} \cdot \bar{Q} + J \cdot K \cdot Q$
 (Q is output from D Flip-Flop)

5.

- a. Ainvert and Binvert should be 1, Operator should be 1
- b. Ainvert and B invert can be 1 or 0 as long as they are both the same. Operator should be 2, CarryIn needs to be zero.